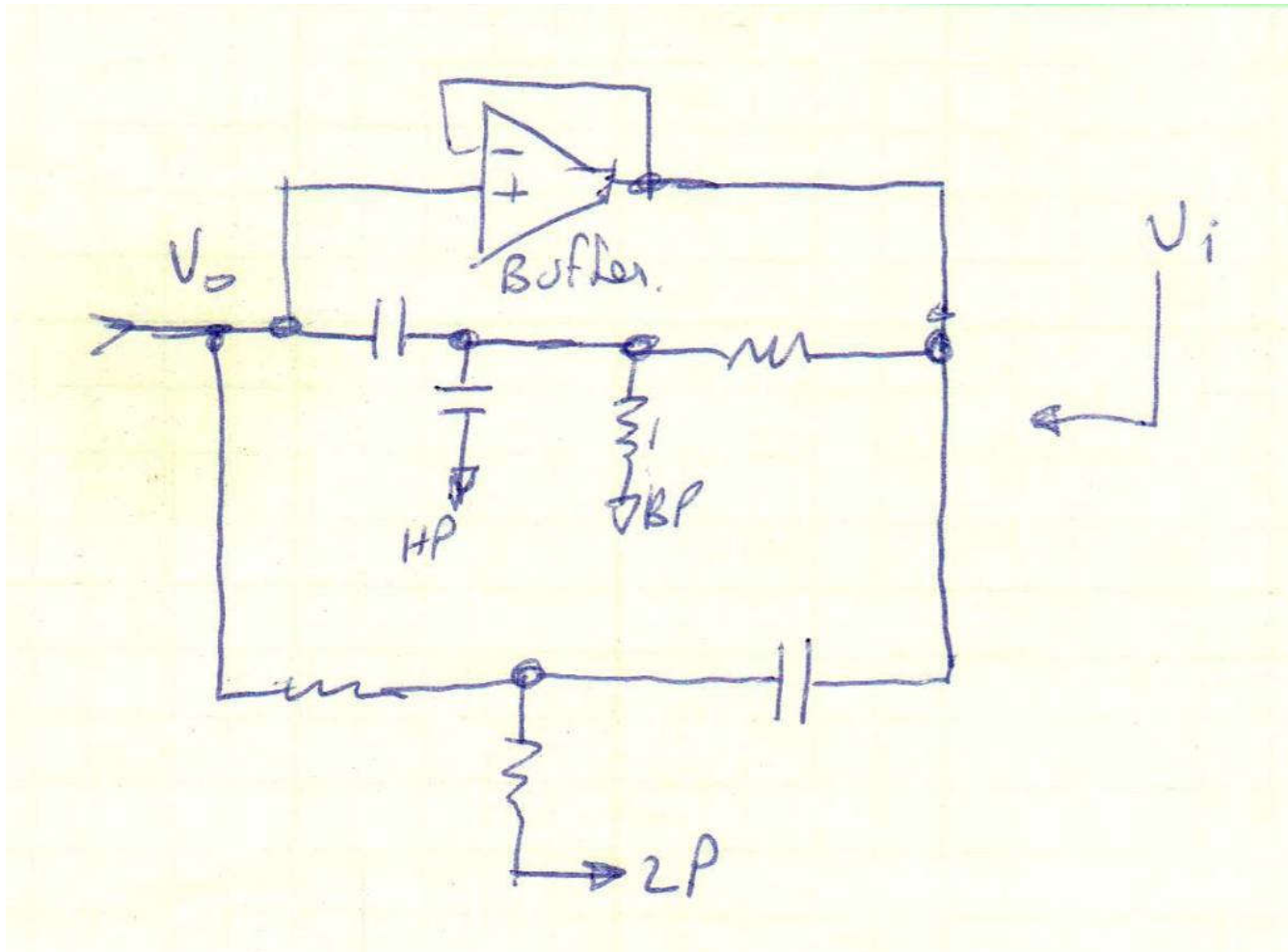




Rako Studios » Media » Tech » Electronics » Simple multi-pass filter

Simple multi-pass filter

One amp yields high-, low-, and band-pass filter functions.



Application engineer Mike Wurtz showed me this simple multi-output filter circuit. It uses one op amp and yields high-pass, low-pass, and band-pass filter functions.

Lede col 2.

Page 2, col 1

Page 2, col 2

Page 3, col 1

Page 3 col 2

Page 4, col 1

Page 4, col 2